

Signal Processing – Analog Part

Submitted To:

Prof. Ulf Witkowski

South Westphalia University of Applied
Sciences

Soest Campus

Presented by,

Md. Saiful Islam Sajol

Matriculation no. 30042836

Task 1

$$\frac{V_1}{V_{in}} = - \frac{R_1 R_3 R_4 + R^2 R_1^2 R_4 s^2 C^2}{R_2 R_3 R_4 + R^2 R_1 R_2 R_4 s^2 C^2 + R R_1 R_2 R_3 s C}$$

➡ Notch (Band Reject Filter)

$$\frac{V_2}{V_{in}} = \frac{R^2 R_1^2 R_3 s^2 C^2}{R R_1 R_2 R_3 s C + R_2 R_3 R_4 + R^2 R_1 R_2 R_4 s^2 C^2}$$


➡ High Pass Filter

$$\frac{V_3}{V_{in}} = \frac{-R R_1^2 R_3 s C}{R R_1 R_2 R_3 s C + R_2 R_3 R_4 + R^2 R_1 R_2 R_4 s^2 C^2}$$


➡ Band Pass Filter

$$\frac{V_4}{V_{in}} = \frac{R_1^2 R_3}{R R_1 R_2 R_3 s C + R_2 R_3 R_4 + R^2 R_1 R_2 R_4 s^2 C^2}$$


➡ Low Pass Filter

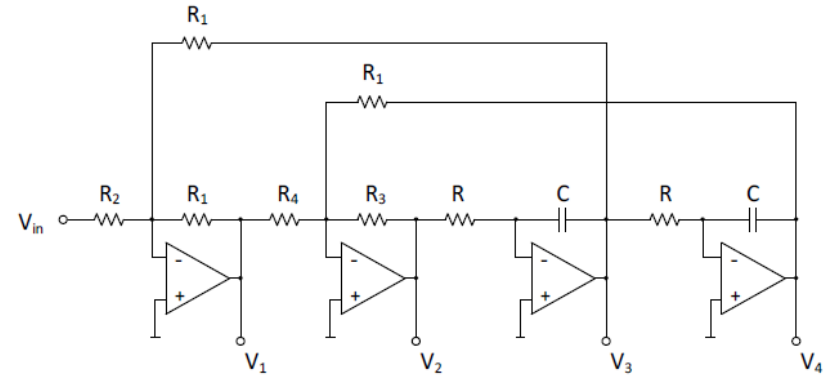


Task 2

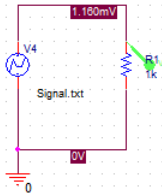

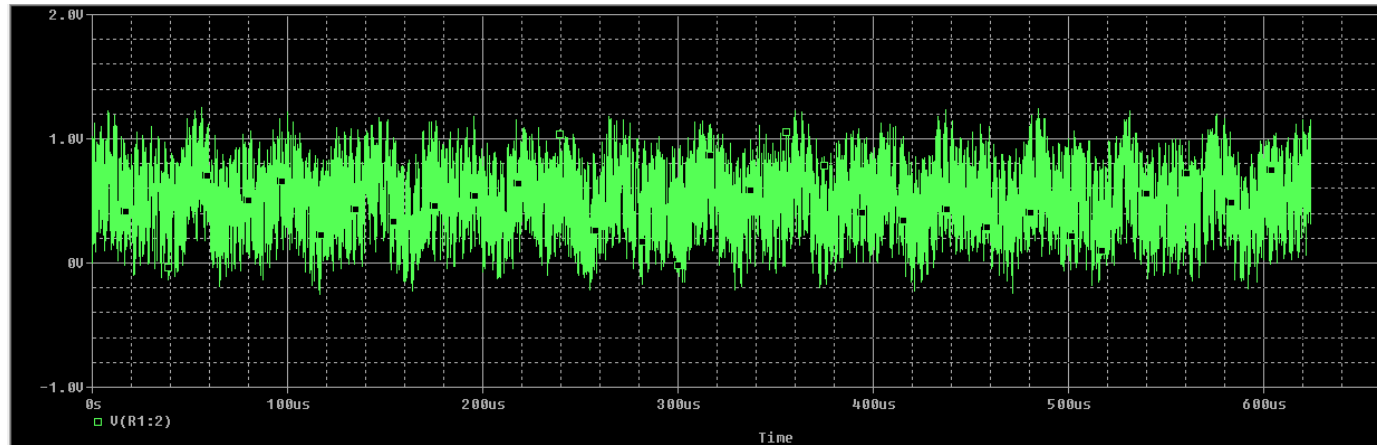voltage source
generating the
noisy signal.






↓ FFT

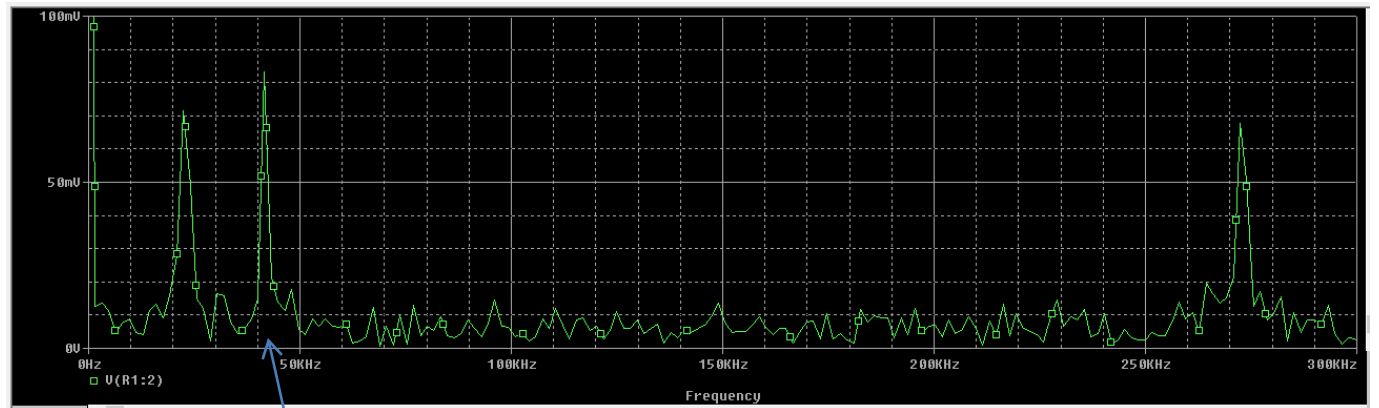

frequency of the wanted
signal, it is $f_{\text{target}} = 42\text{KHz}$

Solution :

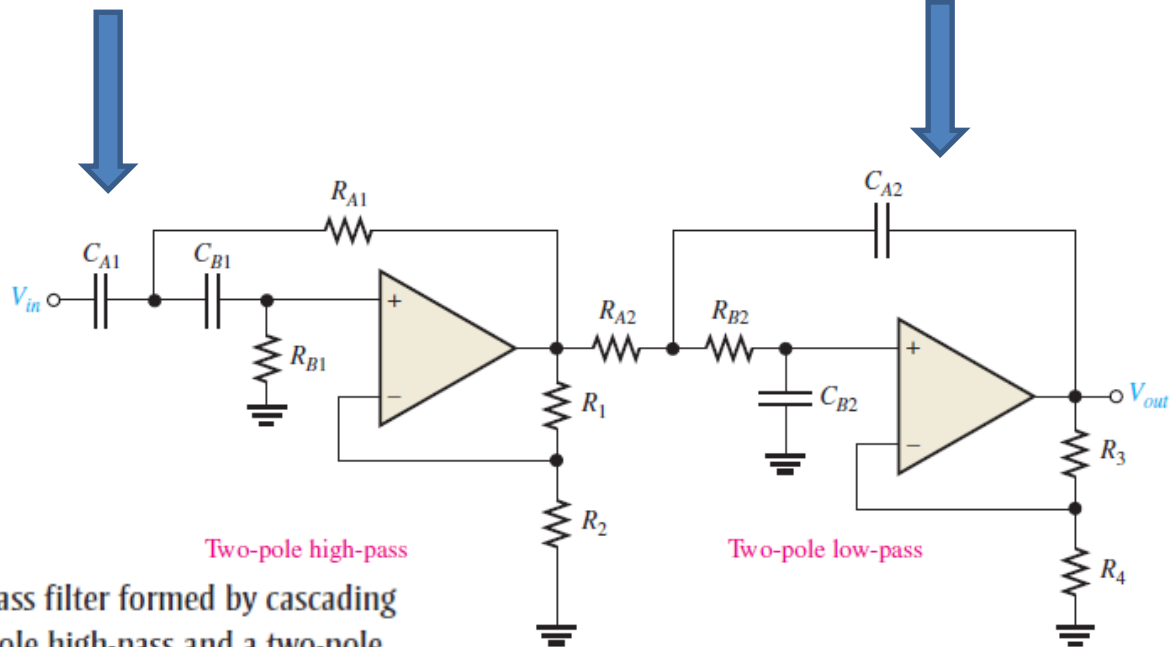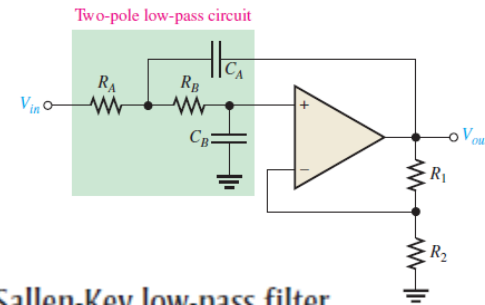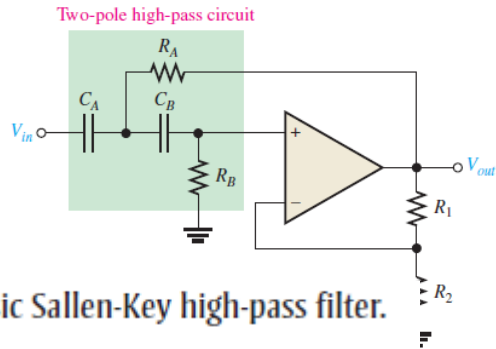

Band-pass filter formed by cascading a two-pole high-pass and a two-pole low-pass filter (it does not matter in which order the filters are cascaded).

$$f_{c1} = \frac{1}{2\pi\sqrt{R_{A1}R_{B1}C_{A1}C_{B1}}}$$

$$f_{c2} = \frac{1}{2\pi\sqrt{R_{A2}R_{B2}C_{A2}C_{B2}}}$$

$$f_0 = \sqrt{f_{c1}f_{c2}}$$

$f_c = 42\text{kHz}$ and $f_{c1} = 39\text{kHz}$ (arbitrary)
 $f_{c2} = f_c^2 / f_{c1} = 42^2 / 39 = 45.23\text{kHz}$
 Bandwidth, $B = (45.23 - 39)\text{kHz} = 6.231\text{kHz}$

Finding parameters of High pass Filter Side

For simplicity,

We select $R_{B1} = R_{A1} = R_2 = 3.9\text{k}\Omega$ (arbitrary)

$F_{c1} = 1 / (2 \cdot \pi \cdot RC)$

$C = 1046\text{pF} \sim 1000\text{pF}$ (E-24 sequence)

$C_{A1} = C_{B1} = C_1 = 1000\text{pF}$

$R_1 / R_2 = 0.586$ (from chart)

$R_1 = 0.586 \cdot 3.9\text{k} = 2.285\text{k}\Omega$

Two-pole high-pass

Two-pole low-pass

Values for the Butterworth response.

ORDER	ROLL-OFF DB/DECADE	1ST STAGE			2ND STAGE			3RD STAGE		
		POLES	DF	R_1/R_2	POLES	DF	R_3/R_4	POLES	DF	R_5/R_6
1	-20	1	Optional							
2	-40	2	1.414	0.586						
3	-60	2	1.00	1	1	1.00	1			
4	-80	2	1.848	0.152	2	0.765	1.235			
5	-100	2	1.00	1	2	1.618	0.382	1	0.618	1.382
6	-120	2	1.932	0.068	2	1.414	0.586	2	0.518	1.482

Finding parameters of Low pass Filter Side

For simplicity,

We select $R_{B2} = R_{A2} = R_4 = 3.9\text{k}\Omega$ (arbitrary)



$F_{c2} = 1 / (2 \cdot \pi \cdot RC)$

$C = 902.25\text{pF} \sim 910\text{pF}$ (E-24 sequence)

$C_{A2} = C_{B2} = 910\text{pF}$

$R_3 / R_4 = 1$ (from chart)

$R_3 = R_4 = 3.9\text{k}\Omega$

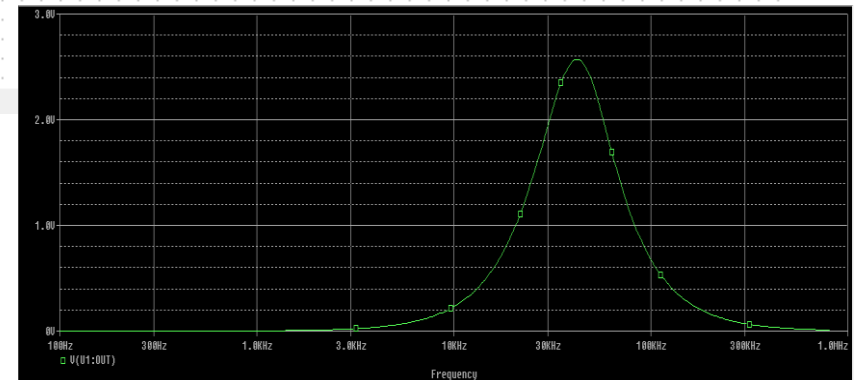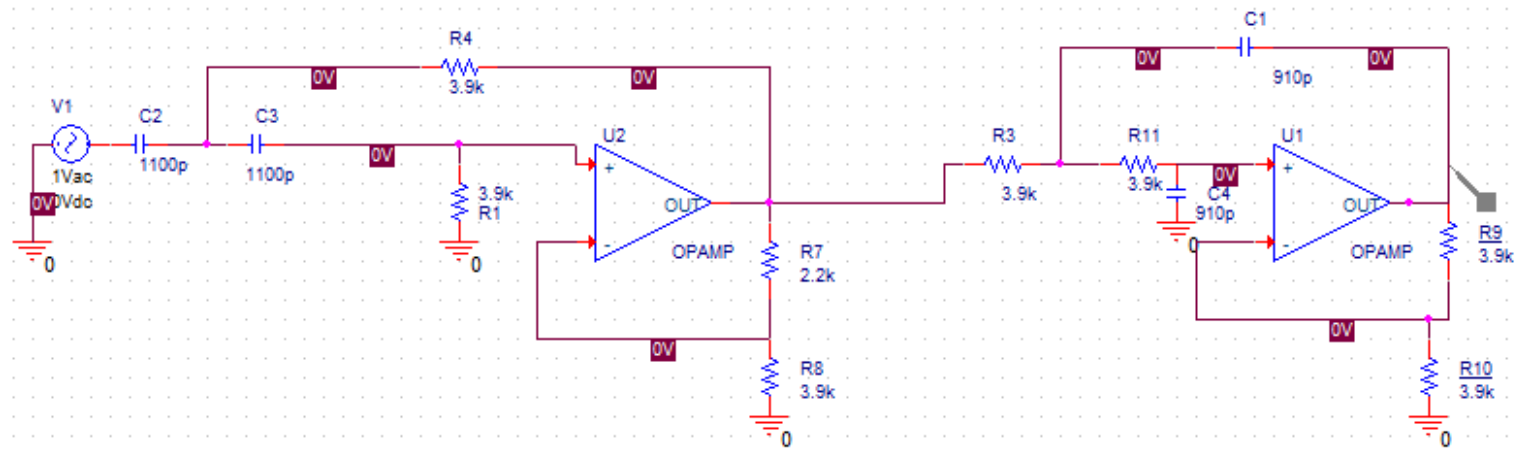

Time Domain

